

KATHMANDU UNIVERSITY
End Semester Examination
January/February, 2024

Level : B.E
Year : II
Time : 2 hrs. 30 mins.

01 FEB 2024

Course : EEEG 214
Semester : II
F. M. : 40

SECTION "B"
[5Q. × 8 = 40 marks]

Attempt *ANY FIVE* questions. Assume suitable data if necessary, Symbol has their usual meaning.

1.
 - a. Derive and discuss the expression for the feedback system. Also, explain Barkhausen Criteria.
 - b. Derive the expression of oscillation frequency and feedback gain for RC bridge oscillator.
2.
 - a. Explain the free running oscillator using transistor circuit, also derive the expression for frequency generation.
 - b. Discuss the operation of full wave precision rectifier.
3.
 - a. What is phase locked loop? List a few applications of PLL. Explain any one application in detail.
 - b. Design an active low pass filter having cut-off frequency of 2 kHz with phase and magnitude plot.
4.
 - a. Derive the expression for maximum fan-out for RTL inverter logic.
 - b. Analyze the circuit of DTL circuit and mention two reasons behind the modification of DTL circuit.
5.
 - a. What are the major steps of the planner process? Discuss the crystal growth in Czochralski process and wafer preparation.
 - b. Fabricate the passive components in a single wafer.
6.
 - a. Explain working principle of 555 timer circuit with the help of its internal blocks.
 - b. Discuss the LC tank circuit. Derive the expression for Colpitts oscillator

